

HOOKUP GUIDE

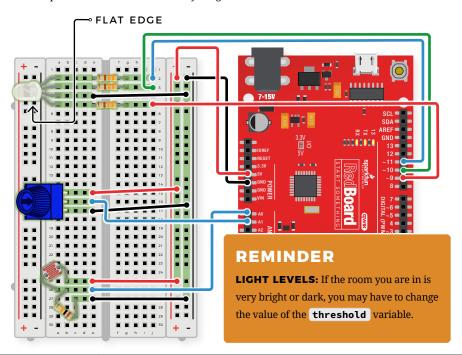READY TO START HOOKING EVERYTHING UP? Check out the circuit diagram and hookup table below to see how everything is connected.



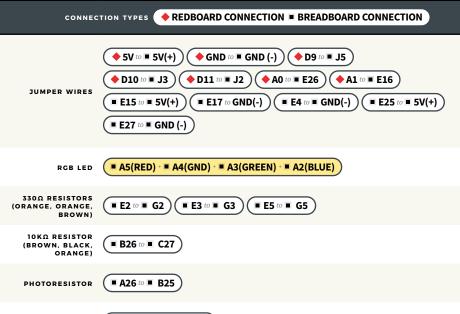

■ B15 + ■ B16 + ■ B17

POTENTIOMETER